

**International Islamic University Chittagong**  
**Department of Electrical and Electronic Engineering**

Final Examination Autumn-2018  
 Course Code: EEE-2407  
 Time: 2 hours 30 minutes

Program: B.Sc. Engg. (EEE)  
 Course Title: Digital Electronics  
 Full Marks: 50

**Part A**


[Answer any two questions from the followings; figures in the right margin indicate full marks.]

- |       |   |   |
|-------|---|---|
| 1(a). | Design a circuit that compares two 2-bit numbers, A and B, to check whether they are equal or unequal. The circuit has three output x,y,z, so that $x=1$ if $A=B$ or $y=1$ if $A>B$ or $z=1$ if $A<B$ . | 3 |
| 1(b). | Explain the main functional difference between a Binary adder and BCD adder with an example.  | 1 |
| 1(c). | Design a BCD adder to add two single digit decimal numbers. Your answer should include the detail design procedure.   | 6 |
| 2(a). | Design a 4-bit binary parallel adder including look ahead carry generator.  | 5 |
| 2(b). | Define decoder. Implement a full-subtractor circuit by means of a decoder.  | 3 |
| 2(c). | Construct a $5 \times 32$ decoder using two $4 \times 16$ decoders.   | 2 |
| 3(a). | Design a Quadruple 2-to-1 line multiplexer.   | 4 |
| 3(b). | Draw the characteristic and excitation tables of RS and JK flip flops.  | 3 |
| 3(c). | Draw the logic diagram of a 'D' & 'T' flip flop using only NAND gates.  | 3 |

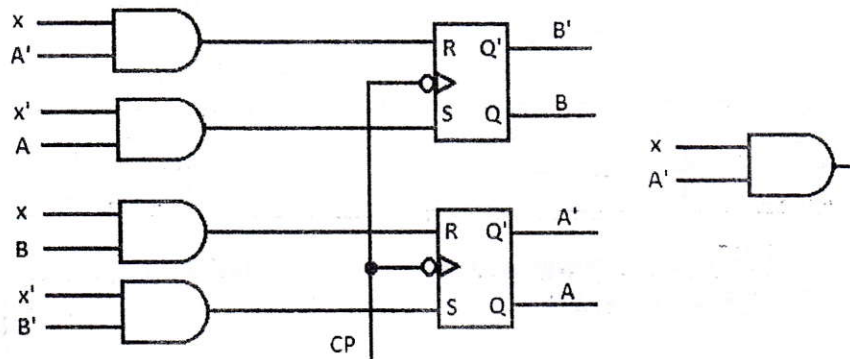**Part B**

[Answer any three questions from the followings; figures in the right margin indicate full marks.]


- 4(a). Draw the state table and state diagram for the following sequential circuit. 6



- 4(b). Design a 3-bit synchronous counter using D flipflop. 4

- 5(a). How two NOR gates can construct a 1-bit memory element? Explain with proper logic diagram. 2
- 5(b). Draw the logic diagram of a JK flip-flop and find out the next state of the flip-flop for the following conditions explaining the operation of the circuit. 4
- Present state  $Q(t)=0$ , Inputs  $J=1$  and  $K=0$ .
  - Present state  $Q(t)=1$ , Inputs  $J=1$ ,  $K=1$ .
- 5(c). Introduce the multiple transition problem in triggering of clocked flip-flops. How this problem can be solved by using a master-slave flip-flop? 4

 - 6(a). Draw a 4-bit serial in/serial out shift register. Also draw the output wave forms for the following data input and the clock waveform if it is fed to the above register. 5



- 6(b). Assume you need to store 8-bit of data in a register. How many clock pulse you will need to load the data and to read the data if the register is a: 2
- Serial in-serial out register
  - Serial in-parallel out register
  - Parallel in-serial out register
  - Parallel in-parallel out register
- 6(c). Draw the sequence table of a 5-bit Johnson counter and its logic diagram. 2

- 7(a). Design a 4-bit serial out shift register. 3
- 7(b). Reduce the states of the following state table and draw the reduced state table and diagram. 4

Present state	Next state		Output	
	x = 0	x = 1	x = 0	x = 1
a	a	d	1	0
b	e	d	0	0
c	a	b	0	1
d	e	f	0	1
e	a	f	0	1
f	g	f	0	1
g	a	f	0	1

- 7(c). Draw the state table for a 3 bit counter and determine the flip-flop inputs if it is to be designed with J-K flip-flop. 3