

International Islamic University Chittagong

Department of Computer Science and Engineering

B. Sc. in CSE

Final Examination-Spring 2023

Course Code: CSE 2323

Course Title: Digital Logic Design

Time: 2 hours 30 minutes

Full Marks: 50


(i) The figures in the right-hand margin indicate full marks

[Answer the questions from the followings. Parts of the same question must be answered serially]

Part A

CO DL Marks

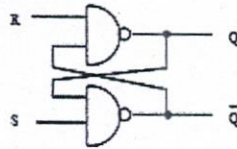1. a) The figure below shows an RS latch made out of NAND gates (rather than NOR gates). How do Q and Q' (Prime) depend on the RS inputs? i.e. verify that the circuit can indeed be used as a RS latch. CO2 A 5



Or, Design a SR Flip Flop using NAND gate.

1. b) What is flip-flop triggering problem? Describe the master-slave D flip. CO1 U 5
2. a) Differentiate between combinational logic and sequential logic. List some applications of sequential logic. What are the major differences between latch and flip? CO1 U 5
2. b) Design a bus system that would take 4-bits input from two input devices namely keyboard and mouse using multiplexer. CO3 A 5

Or, How does JK flip-flop remove the indeterminate states of S-R flip-flop? Design a JK flip-flop and show its characteristic equation, characteristic table, logic diagram and timing diagram.

Part B

3. a) Design the sequential circuit described by the following state equations using JK flip-flops. CO2 A 5
 $A(t+1) = xAB + yA'C + xy$
 $B(t+1) = xAC + y'BC'$
 $C(t+1) = x'B + yAB'$
3. b) Design BCD counter with proper timing diagram. CO3 A 5
4. a) Design a 4-bit Up counter with T flip-flop. CO2 A 5
4. b) What are the basic difference between ring counter and Johnson counter? Explain with Block diagram. CO3 R 5
5. a) Using sequence generator generates sequence of 11010 and also draw proper circuit diagram. CO2 A 5

Or, Design a multiplexer using the following Boolean Equation.

$$F(A, B, C) = \sum (1, 3, 4, 5, 6, 7)$$

5. b) If counter is having 10FF. It is initially 0. What count will it hold after 2060 pulses? Design D latch with truth table and proper circuit diagram. CO2 A 5
- Or, What is a memory cell? Design a 4x4 RAM and describe its operation with example.