

# International Islamic University Chittagong (IIUC)

## Dept. of Electronic and Telecommunications Engineering

Final Examination, Autumn 2018

Course Code: ETE 2323

Course Title: Digital Electronic & Logic Design

Full Marks: 50

Time: 2.5 Hours

### [Part- A]

[Answer any two of the following questions]

1. a) Interpret how Karnaugh map is simple straightforward procedure for minimizing Boolean functions? Build up Karnaugh maps for 5 variables Boolean functions. 3+3
- b) Using K-map method, simplify the Boolean function 4  
 $F(A,B,C,D) = \sum(2,3,4,5,6,7,9,10,12,13,14,15)$
2. a) Differentiate between Half Adder and Full Adder Circuit. Formulate the logical expressions output Sum and Carry for a full Adder circuit. 2+4
- b) Using the block diagram method, implement the following function using only NAND gates. 4  
 $F = AB + CD + E$
3. a) Write down the necessity of parity generator and checker logic circuit during the transmission of binary information. 4
- b) Design a combinational circuit to generate and check for even parity of three bits binary message code. 6

### [Part- B]

[Answer any three of the following questions]

4. a) Discuss a technique (principle of look-ahead carry) with suitable example which minimizes the carry propagation delay in the binary parallel adder circuit. 4
- b) Design a Decimal Adder by using two 4 bit Full Adder Circuits. 6
5. a) Differentiate between Decoder and Encoder Circuit. 4
- b) Design a full adder circuit by using Decoder and OR gates. 6

6. a) Implement the following function with a multiplexer, 5  
$$Y(A, B, C, D) = \sum(1,2,3,6,8,11,13,14)$$
 consider the variable A in the multiplexer input and B, C, D to the selection lines of an  $8 \times 1$  MUX.
- b) Design a combinational circuit using a ROM. The circuit accepts a 3-bit binary number and generates an output binary number equal to the square of input. 5
7. a) What is counter? Using D-type flip flop, design a 2 bit binary counter using sequence 0,1,2,3 and repeat. 4
- b) Show the logic diagram and characteristic table for JK flip-flop. Determine it's characteristic equation. 6