

International Islamic University Chittagong
Department of Electrical and Electronic Engineering

Final Examination Autumn-2018
 Course Code: EEE-2411
 Time: 2 hours 30 minutes

Program: B.Sc. Engg. (EEE)
 Course Title: Electronics II
 Full Marks: 50

Part A

[Answer any two questions from the followings; figures in the right margin indicate full marks.]

- 1(a). Explain the operation of Wien bridge oscillator and calculate its frequency of oscillation. 4
- 1(b). What is oscillator? Write down the conditions that must be maintained to produce an oscillation. 2
- 1(c). Explain the operation of Phase shift oscillator and calculate its frequency of oscillation. 4
- 2(a). In an ac amplifier, which capacitors affect the low-frequency gain? How is the high-frequency gain of an amplifier limited? 2
- 2(b). The bypass RC circuit is formed by C_2 and the resistance looking in at the emitter, $R_{in(emitter)}$, as shown in Fig. 2.1. Derive $R_{in(emitter)}$ with proper diagrams. 5

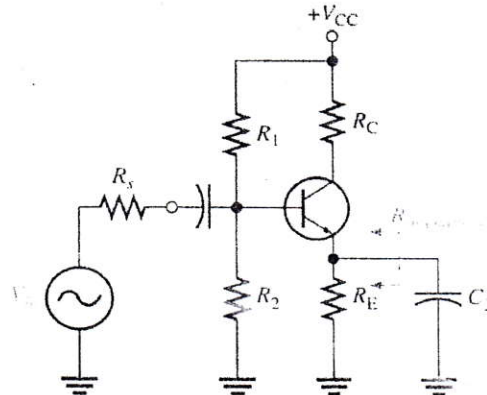


Fig. 2.1

- 2(c). The midrange voltage gain of a certain amplifier is 200. The input RC circuit has a lower critical frequency of 1 kHz. Determine the actual voltage gain at $f = 1$ kHz, $f = 100$ Hz, and $f = 10$ Hz. 3
- 3(a). Define the term : (i)Decibel (ii) Bode plot 2
- 3(b). Explain the operation of astable multivibrator using 555 timer. 5
- 3(c). Determine the amplitude and frequency of the saw tooth output in Fig-3.1 (see page 2). 3
 Assume that the forward PUT voltage, V_F is 1V. Also sketch the output waveform.

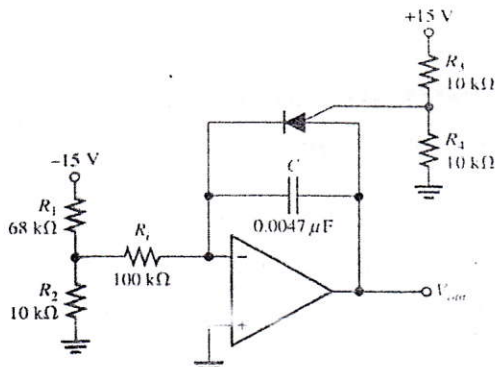


Fig. 3.1

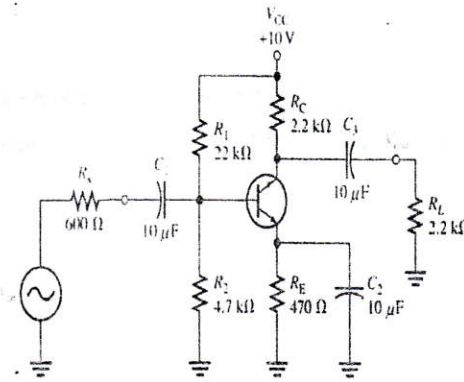


Fig. 4.1

Part B

[Answer any three questions from the followings; figures in the right margin indicate full marks.]

- 4(a). Derive the equivalent high-frequency input RC circuit for the BJT amplifier in Fig. 4.1 (above). Use this to determine the upper critical frequency due to the input circuit. The transistor's datasheet provides the following: $\beta = 120$, $C_{be} = 20 \text{ pF}$ and $C_{bc} = 2.4 \text{ pF}$. 5
- 4(b). What is Bandwidth? What is the bandwidth of an BJT amplifier when $f_{cu(dom)} = 25 \text{ kHz}$ and $f_{cl(dom)} = 100 \text{ Hz}$? 2
- 4(c). What determines the frequency response of an amplifier? A certain amplifier has $f_{cu(input)} = 3.5 \text{ MHz}$ and $f_{cu(output)} = 8.2 \text{ MHz}$. Which circuit dominates the high-frequency response? 3
- 5(a). What limits the passband of an active high-pass filter? 2
- 5(b). What is the primary purpose of cascading low-pass filters? Draw the circuit diagram of a third order low pass filter. 2
- 5(c). Determine the center frequency, maximum gain, and bandwidth for the filter in Fig. 5.1 given below. 5


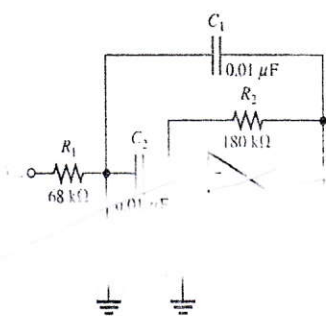


Fig. 5.1

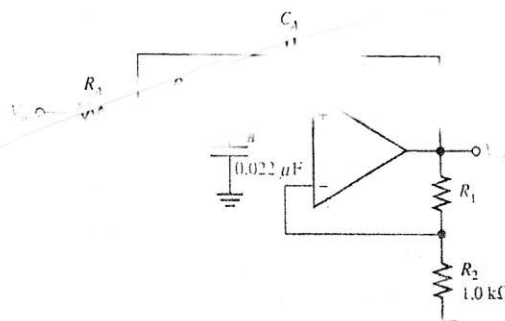

- 6(a). Describe the construction and working principle of a solar cell. 6
- 6(b). Write short notes on the following: Any two 4
 (i) Photo diode (ii) LED (iii) Photo conductive cell
- 7(a). What determines the high-frequency response of an amplifier? Draw the circuit diagram of High-frequency equivalent circuit after applying Miller's theorem. 3
- 7(b). Name the basic parts of an active filter. If three two-pole high-pass filters and one single-pole high-pass filter are cascaded, what is the resulting roll-off? 3
- 7(c). Determine the critical frequency of the Sallen-Key low-pass filter in Fig. 7.1 given above, and set the value of for an approximate Butterworth response. 4