

International Islamic University Chittagong

Department of Electrical and Electronic Engineering

Final Assessment of Autumn-2020

Course Code: **EEE-2407**

Time: **5 hours** (Writing- **4 hours 30 minutes** + **30 minutes** submission time)

Program: B.Sc. Engg. (EEE)

Course Title: **Digital Electronics**

Full Marks: **50** (Written 30 + Viva/Viva-Quiz-20)


[Answer **each of the** questions from the followings; Figures in the right margin indicate full marks. **Answer script must be submitted through online method within 5 hours from starting time.**]

- 1(a).** Draw the logic diagram of a look-ahead carry generator for a 3-bit full adder. **CO4 C 02**
- 1(b).** Design a 3-bit Encoder and find its truth table. How can you transform an Encoder into a Multiplexer? **CO3 U 02**
- 1(c).** Design the following function with a 5x32 decoder IC: **CO4 Ap 02**
 $F(A,B,C,D,E) = \sum (X, Y, 12, 15, 19, 24, 27, 30, 31)$
 [Take X and Y from last two digit of your ID, e.g. ET1830XY. If X=Y, take only one]
- 2(a).** Implement the following boolean function with multiplexer: **CO4 Ap 03**
 $F(A,B,C,D) = \sum (X,Y,6,7,9,11,14,15)$, take C as input line.
 [Take X and Y from last two digit of your ID, e.g. ET1830XY. If X=Y, take only one]
- 2(b).** Construct a BCD to Excess-3 code converter using: **CO4 C 02**
 i) Binary parallel adder IC
 ii) Decoder
- 2(c).** Draw the logic diagram of all basic flip-flops using only NAND gates. **CO3 C 01**
- 3(a).** Design the logic diagram of the sequential circuit that corresponds with the following state table **CO5 C 04**

Present state	Input	Next state	Output
A B C	x	A B C	y
0 0 0	0	0 0 1	0
0 0 0	1	1 1 1	1
0 0 1	0	1 1 0	0
0 0 1	1	1 1 1	0
0 1 1	0	0 0 0	0
0 1 1	1	0 1 1	1
1 1 0	0	0 0 0	1
1 1 0	1	0 1 1	0
1 1 1	0	1 1 0	0
1 1 1	1	0 0 1	1

3(b). Derive the state table from the following state diagram.

CO5 An 02

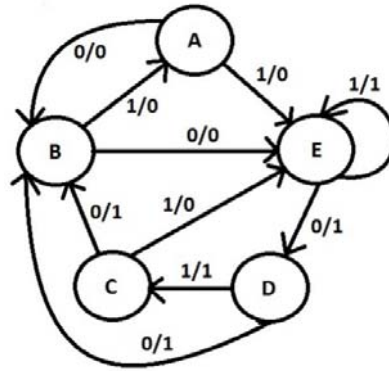

4(a). Construct a 3-bit parallel in-serial out shift register. Explain how it works. **CO5 C 03**

4(b). Assume you need to store 16-bit of data in a register. How many clock pulse you will need to load the data and to read the date if the register is a: **CO5 An 01**

- (i) Serial in-serial out register
- (ii) Serial in-parallel out register
- (iii) Parallel in-serial out register
- (iv) Parallel in-parallel out register

4(c). Draw the sequence table of a 7-bit Ring counter and its logic diagram. Explain how this counter works. **CO5 C 02**

5(a). Design a 7-bit Asynchronous up counter that can count from 0-XY, where X and Y are last two digits of your ID, e.g. ET1830XY. **CO5 C 03**

5(b). Design a synchronous BCD counter. **CO5 An 02**

5(c). What is MOD number? How to find the frequency of the output signal of the last flip-flop for an asynchronous counter? **CO3 R 01**

6. Viva/Viva-Quiz: The time of viva/viva-quiz will be declared in google classroom. **20**

Shafait Ahmed
Asst. Prof.