

**International Islamic University Chittagong**  
**Department of Electrical and Electronic Engineering**

<b>Final Assessment Autumn 2020</b>		Program: B.Sc. Engg. (EEE)			
Course Code: <b>EEE 4801</b>		Course Title: <b>Power System Protection</b>			
Time: 5 hours (Writing - 4 hours 30 minutes + 30 minutes submission time)		Full Marks: 50 (Written 30 + Viva/Viva-Quiz-20)			
[Answer each of the questions from the followings; Figures in the right margin indicate full marks. Answer script must be submitted through online method within 5 hours from starting time. Also, write down the Q. Set on the front page of your answer script]					
<b>Q. Set-B</b>					
<b>1(a).</b>	According to constructional feature, which circuit breaker is smaller than other circuit breaker? Describe its operation with proper sketch.	<b>CO2</b>	<b>R</b>		3
<b>1(b).</b>	An air blast circuit breaker is designed to interrupt a transformer magnetizing current of <b>XXA</b> (r.m.s) chops the current at an instantaneous value of 7A. If the values of L and C in the circuit are 35.2H and 0.0023uF, find the value of voltage that appears across the contact of the breaker. Assume that all the inductive energy is transferred to the capacitance. <b>XX</b> is the 1 <sup>st</sup> two digits of your ID.	<b>CO2</b>	<b>E</b>		1
<b>1(c).</b>	Discuss different types of circuit breaker contact point.	<b>CO1</b>	<b>U</b>		2
<b>2(a).</b>	Which types of protection can be possible using Buchholz relay for transformer protection? Describe its operation with proper sketch.	<b>CO2</b>	<b>An</b>		3
<b>2(b).</b>	A three-phase transformer of <b>xxx/zzzz</b> line volt is connected in star/delta. The protective transformers on 220V side have a current ratio of 500/5. What should be the CT ratio of 11000V side? <b>xxx</b> is the 1 <sup>st</sup> three digits of your ID and <b>zzzz</b> is the last four digits of your ID.	<b>CO1</b>	<b>E</b>		2
<b>2(c).</b>	Draw the schematic diagram of earth fault protection of transformer.	<b>CO1</b>	<b>R</b>		1
<b>3(a).</b>	How many protections can be possible using modified differential protection of alternator. Discuss with proper sketch.	<b>CO2</b>	<b>U</b>		4
<b>3(b).</b>	A star connected, 3-phase, <b>YYMVA</b> , <b>R.R</b> kV alternator s protected by circulating current protection, the star point being earthed via a resistance r. Estimate the value of earthing resistor if 85% of the stator winding is protected against earth fault. Assume an earth fault setting of 25%. Neglect the impedance of the alternator winding. <b>YY</b> is the 1 <sup>st</sup> two digit of your ID and <b>R.R</b> is the 1 <sup>st</sup> two digit of your ID	<b>CO3</b>	<b>E</b>		2
<b>4.</b>	Discuss the operation of different types of time graded overcurrent protection for 33kV line. Which system is more effective comparing to those systems?	<b>CO2</b>	<b>U,An</b>		6
<b>5(a).</b>	For designing a numerical relay, which features should be considered?	<b>CO1</b>	<b>An</b>		2
<b>5(b).</b>	For designing a 11kV line protection system, what will be the arrangements of numerical relay?	<b>CO3</b>	<b>U</b>		2
<b>5(c).</b>	Discuss different types of lightening stroke.	<b>CO1</b>	<b>R</b>		2
<b>6.</b>	Viva/Viva-Quiz: The time of viva/viva-quiz will be declared in google classroom.				<b>20</b>