

**International Islamic University Chittagong**  
**Department of Electrical and Electronic Engineering**

**Assignment Autumn-2020**

**Course Code: EEE-4807**

**Program: B.Sc. Engg. (EEE)**

**Course Title: High Voltage Engineering**


**Full Marks: 30**

[Answer **each of the** questions from the followings; Figures in the right margin indicate full marks. **write down the Q. Set on the front page of your answer script.**]

**Q. Set-A**

- |              |  |            |              |           |
|--------------|--|------------|--------------|-----------|
| <b>1(a).</b> | Explain the operation of a simple voltage doubler circuit used for generation of high DC voltages.   | <b>CO1</b> | <b>U</b>     | <b>02</b> |
| <b>1(b).</b> | Derive the expression for ripple and regulation in a voltage multiplier circuits. How are the ripple and regulation minimized?   | <b>CO1</b> | <b>An</b>    | <b>03</b> |
| <b>1(c).</b> | A ten-stage Cockraft-Walton circuit has all capacitors of $0.06\ \mu\text{F}$ . The secondary voltage of the supply transformer is 100 kV at a frequency of 150Hz. If the load current is 1 mA, Determine,<br>i. Voltage regulation<br>ii. The optimum number of stages for maximum output voltage | <b>CO2</b> | <b>Ev</b>    | <b>02</b> |
| <b>2(a).</b> | How are damped high-frequency oscillations obtained from a Tesla coil?   | <b>CO1</b> | <b>An</b>    | <b>02</b> |
| <b>2(b).</b> | Draw the equivalent circuit of a three-stage Cascaded transformer and determine the expression for short circuit impedance of the transformer.   | <b>CO1</b> | <b>R, Ev</b> | <b>03</b> |
| <b>2(c).</b> | A 100KVA, 250V/200kV testing transformer has resistance and reactance of 1% and 10% respectively. It is used to test a capacitive sample at 600KV, and at 0.3Amp. Determine the series Inductance required. Frequency = 55Hz. Assume a suitable value for resistance of the inductor coil.         | <b>CO2</b> | <b>Ev</b>    | <b>02</b> |
| <b>3(a).</b> | Draw the voltage wave shape of lightning impulse and explain it in detail. Also, define the different standard of impulse voltage.   | <b>CO1</b> | <b>R</b>     | <b>02</b> |
| <b>3(b).</b> | An impulse generator has eight stages with each condenser rated for $0.16\ \mu\text{F}$ and 125 kV. The load capacitor available is 1000 pF. Calculate, the series resistance, and the damping resistance needed to produce $1.2/50\ \mu\text{s}$ is an impulse wave.                              | <b>CO2</b> | <b>Ev</b>    | <b>02</b> |

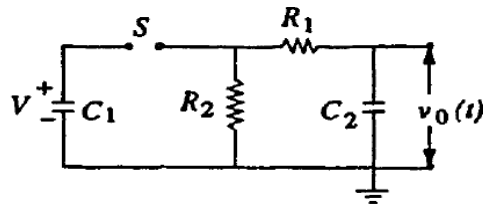- 3(c). Give a complete analysis of the impulse circuit shown in “Fig: 01” and derive the condition for physical Realization of wave front and wave tail resistances. **CO1 An 03**



“Fig: 01” Impulse Generator Circuit.

**Assignment: 21 Marks**

**Viva/Quiz based on Assignment: 9 Marks (Quiz)**

**Total: 30 Marks**