

International Islamic University Chittagong

Department of Computer Science and Engineering

B. Sc. in CSE

Final Exam, Spring-2023

Course Code: **EEE-1121**

Time: 2 hours 30 minutes

Course Title: **Basic Electrical Engineering**

Full Marks: 50

The figures in the right-hand margin indicate full marks

Part A

[Answer the questions from the followings]

1. a) What is a waveform? Demonstrate some waveforms with proper diagram. C01 Ap 3
1. b) Find the phase angle between $i_1 = -4 \sin(377t + 25^\circ)$ and $i_2 = 5 \cos(377t - 40^\circ)$, does i_1 lead or lag i_2 ? C03 E 3
1. c) Find the rms value of the signal shown in below Fig. 1(c) C03 An 4

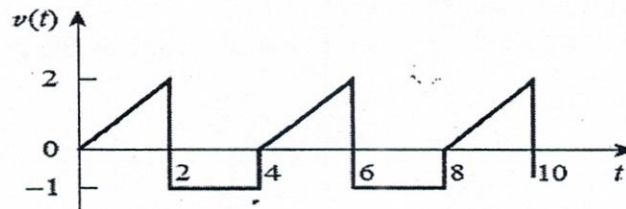


Fig. 1(c)

2. a) Refer to Fig. 2(a) below, determine $v(t)$ and $i(t)$. C04 An 5

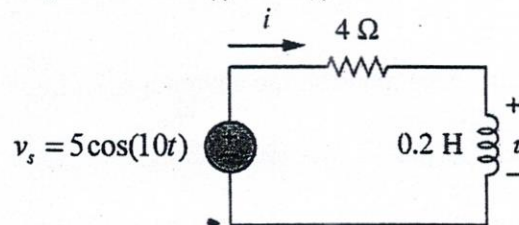


Fig. 2(a)

OR

Solve for I in the following circuit of Fig. 2(a-or)

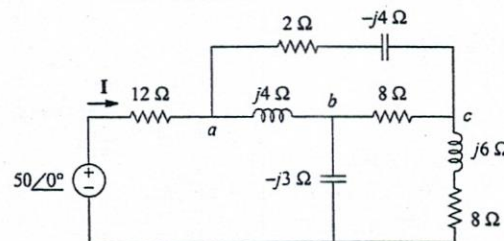


Fig. 2(a-or)

2. b) The voltage across $1 \mu\text{F}$ capacitor is $v = 30 \sin 400t$. What is the sinusoidal expression for the current. Sketch the v and i curves. C03 An 5

OR

What is the voltage and current relation in a capacitive circuit? Explain your answer mathematically.

Part B

[Answer the questions from the followings]

3. a) Design a High pass filter with proper circuit diagram and explain its output characteristics C04 C 5
3. b) Given that $R=20k$, $C=120pF$ sketch the phase plot for both high-pass and low-pass filter and determine the magnitude and phase of $A_v=(V_o/V_i)$ at $f=0.5 f_c$ C04 An 5
4. a) What is the significance of power factor in electrical systems and why is it important to maintain a high power factor? C01 E 3

OR

Calculate the instantaneous power and average power absorbed by a passive linear network if: $v(t)=80 \cos(10t+20^\circ)$ and $i(t)=15 \sin(10t+60^\circ)$.

4. b) Explain what does the power triangle represent and how is it related to the concepts of real power, reactive power, Apparent power? C03 U 3
4. c) In the following circuit calculate the average power absorbed by the resistor and inductor. C03 An 4

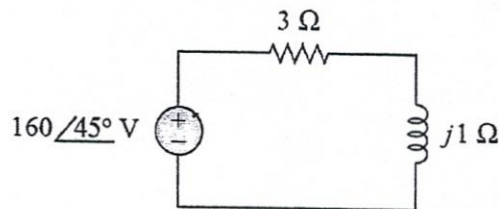


Fig. 4(c)

5. a) Write about three phase system. Also mention the advantages of implementing three phase electrical power system. C01 Ap 3
5. b) Given that $V_{bn}=220 \angle 40^\circ$ Find V_{an} and V_{cn} assuming a negative phase sequence C03 Ap 3

OR

Illustrate four different configurations of three phase balanced system.

5. c) Calculate the line and phase currents from the given system below: C03 An 4

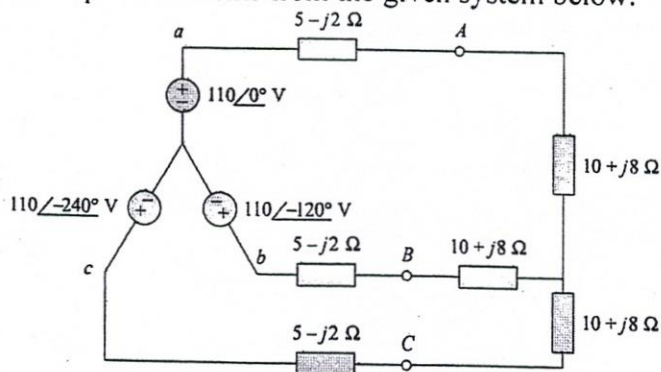


Fig. 5 (c)

OR

A balanced abc -sequence Y-connected source with $V_{an}=100 \angle 10^\circ$ is connected to a Δ -connected load $(8+j4) \Omega$ per phase. Calculate the phase Currents.