

**International Islamic University Chittagong (IIUC)**  
**Department of Electronic and Telecommunication Engineering**  
**Midterm Exam**

Program: B.Sc (Engg.)  
 Course Code: ETE-2341  
 Total Marks: 30

Semester: Autumn2024  
 Course Title: Analog Electronics  
 Time: 1.5Hours

*[(i) Answer all the questions. The figures in the right-hand margin indicate full marks.]*

*[(ii) Course Learning Outcomes (COs) and Bloom's Levels are mentioned in additional Columns.]*

Course Outcomes (COs) of the Questions						
<b>CLO1</b>	Acquire profound knowledge of operational amplifier, oscillator, multi-vibrator and power amplifier related theory and application.					
<b>CLO2</b>	Construct and test different types of operational amplifier circuits and measure their gain and frequency response in a group.					
<b>CLO3</b>	Design basic electronics project based on amplifier					
<b>CLO4</b>	Apply the necessary learning skills in Electronics industries					
Bloom's Levels of the Questions						
Letter Symbols	R	U	Ap	An	E	C
Meaning	Remember	Understand	Apply	Analyze	Evaluate	Create

- Q1. (a) What is feedback circuit? explain the types of feedback circuit. 03 CLO1 U  
 (b) Explain the operation of Emitter circuit follower. 04 CLO1 An  
 (c) With a negative voltage feedback, an amplifier gives an output of 10 V with an input of 0.5 V. When feedback is removed, it requires 0.25 V input for the same output. Calculate 03 CLO1 E  
 (i) gain without feedback (ii) feedback fraction mv.
- Q2. (a) Discuss how get the undamped oscillation from a tank circuit . 03 CLO1 An  
 (b) Write the operation of Tuned Collector circuit 04 CLO1 R  
 (c) In the phase shift oscillator shown in Fig. 14.17,  $R_1 = R_2 = R_3 = 1M\Omega$  and  $C_1 = C_2 = C_3 = 68 \text{ pF}$ . At what frequency does the circuit oscillate ? 03 CLO1 E
- OR
- Q2. (a) Briefly discuss about Oscillatory circuit . 03 CLO1 U  
 (b) Write short notes : 04 CLO1 R  
 (i) Wein Bridge Oscillator  
 (ii) RC Oscillator  
 (c) The ac equivalent circuit of a crystal has these values:  $L = 1H$ ,  $C = 0.01 \text{ pF}$ ,  $R = 1000 \Omega$  and  $C_m = 20 \text{ pF}$ . Calculate  $f_s$  and  $f_p$  of the crystal. 03 CLO1 Ap
- Q3. (a) Write the circuit and operation of Collector Coupled Astable multivibrator. 05 CLO1 An  
 (b) Draw 555 Timer IC block diagram and write important features. 05 CLO1 Ap