

Bismillahir Rahmanir Rahim

# International Islamic University Chittagong (IIUC)

## Department of Computer and Communication Engineering

### Midterm Examination

Program: **B.Sc. (Engg.)**  
Course Code: **CCE-1103**  
Total Marks: **30**

Semester: **Autumn 2022**  
Course Title: **Basic Electrical Engineering**  
Time: **1 Hours 30 Minutes**  
Date: **27/09/2022**

(i) Answer all the questions. The figures in the right-hand margin indicate full marks.

(ii) Course Learning Outcomes (CLOs) and Bloom's Levels are mentioned in additional Columns.

#### Course Learning Outcomes (CLOs) of the Questions


- CLO1** Understand the concepts of basic Circuit element, basic circuit, and basic circuit Laws and magnetic circuit laws.
- CLO2** Introduce series parallel circuit and different network theorem to analysis the circuits.

#### Bloom's Levels of the Questions


Letter Symbols  
Meaning

| R        | U          | Ap    | An      | E        | C      |
|----------|------------|-------|---------|----------|--------|
| Remember | Understand | Apply | Analyze | Evaluate | Create |

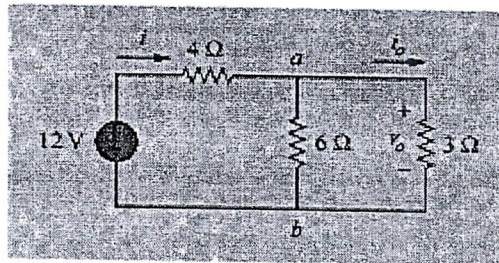
- Q1. a) What do you mean by **1volt** and **1ampere** of current? CLO1 R 2
- b) "Every potential difference is not an emf and vice-versa"—Justify the statement. CLO1 E 4
- c) Find  $i_o$  and  $v_o$  in the circuit given below and also calculate the **power dissipated** in the  $3\text{-}\Omega$  resistor. CLO1 Ap 4



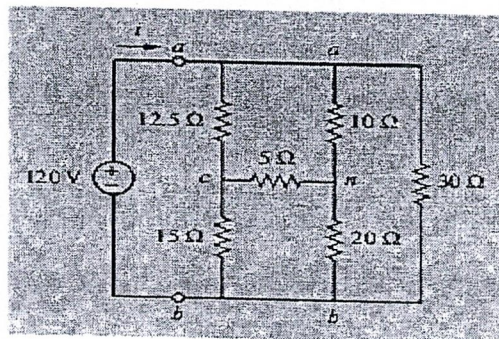
- Q2. a) Derive an expression for equivalent resistances of a **star connected** network to transform into a **delta connected** network. CLO1 Ap 5
- b) Using the expression found above in 'a', obtain the **equivalent resistance  $R_{ab}$**  for the circuit given below and use it to find current  $i$ . CLO1 Ap 5



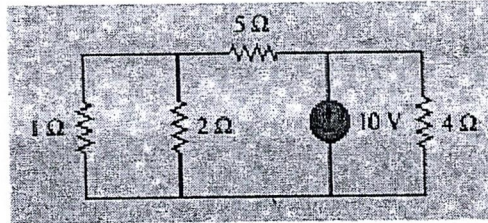- Q3. a) Define – **Node, Branch and Loop** and determine how many branches and nodes does the given circuit have? CLO1 R, E 5




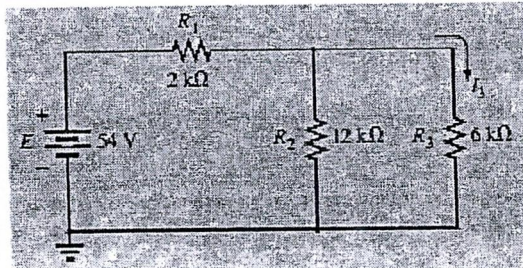- b) Find **current  $I_3$**  for the series-parallel network in the figure given below. CLO2 Ap 5




OR

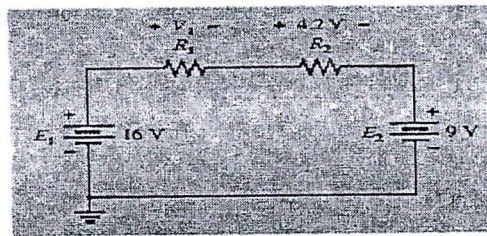- Q3. a) State KCL and KVL and Use Kirchhoff's voltage law to determine the **unknown voltage** for the circuit given below - CLO1 R, E 5



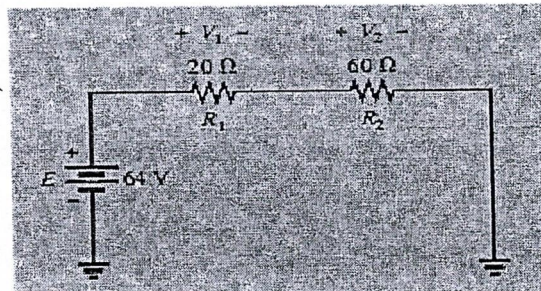- b) For the series circuit given below - CLO2 U, Ap 5
- Without making any calculations, how much larger would you expect the voltage across  $R_2$  to be compared to that across  $R_1$ ?
  - Find the voltage  $V_1$  using only the voltage divider rules.
  - Using the conclusion of part (I), determine the voltage across  $R_2$ .
  - Use the voltage divider rule to determine the voltage across  $R_2$ , and compare your answer to your conclusion in part (III).



**\*\*\* Good Luck \*\*\***