

International Islamic University Chittagong

Department of Computer Science & Engineering

Semester: 3rd

Program: B.Sc. in CSE Semester: 3rd

Session: Spring-2023

Mid Term Examination, Spring-2023

Course Code: CSE-2323

Course Title: Digital Logic Design

Time: 1-Hour 30 minutes

Total Marks: 30

Qns. Each qns. Answer the following Three (3) questions. Each question carries 10 marks.

Question : 1	<p>a. Write down the advantages of digital systems over analog systems with proper example. 2</p> <p>b. Define redundancy theorem with proper example. 2</p> <p>c. Define Positive and negative logic with truth table. 2 “Excess-3 code is self-complementary code “ Is it true or false? Justify your comment.</p> <p>d. Compare between BCD Code and Binary numbers. 1+2=3 Mentioned the rules applied for BCD Addition.</p> <p>e. Just one lines, write down the limitations of BCD Addition. 1</p>
Question : 2	<p>a. How can we identify whether a code is self-complementary or not? Explain with proper example. 2+1+2=5 Write down major properties of Gray Code. Convert 10110110 Gray Code into Binary Code. Or</p> <p>a. If we have,4 inputs NAND Gate then how many 2 input NAND Gates are required to implement it? 2+3=5 Boolean expressions to NAND Gate implementation: $Y=A\bar{+}BC\bar{}$ ($\bar{}$ means Complement)</p> <p>b. What are the key features of Karnaugh map? Solve the following using Karnaugh Map: 5 $F(A,B,C,D,E)=\sum_m(0,1,6,7,8,9,21,22,23,29,31)$</p>
Question : 3	<p>a. Mention the rules for designing combinational circuit with proper example. 3 Or.</p> <p>a. What are the necessary conditions for check board configuration? Justify it with Full Adder Circuit. 3</p> <p>b. Construct a Half Adder using NAND gates. 2</p> <p>c. Explain 2 bit comparator with proper circuit diagram. 2</p>

enclosed in bracket () N.B: The meanings of symbol enclosed in bracket ($\bar{}$) is complement.
 The End**** ****The End****