

International Islamic University Chittagong
Department of Electrical and Electronic Engineering

Final Assignment Test Autumn-2020
 Course Code: **EEE-2301**
 Time: **5 hours** (Writing- **4 hours 30 minutes** + **30 minutes** submission time)

Program: B.Sc. Engg. (EEE)
 Course Title: **Electronics-I**
 Full Marks: **50** (Written 30 + Viva/Viva-Quiz-20)


[Answer each of the questions (1-5) from the followings; Figures in the right margin indicate full marks.]

Don't blindly copy any answer from book/internet/friend. There is serious penalty for plagiarism. A straight zero will be given for the cause. Please write from your own understanding.

Question Distribution Procedure	
Last Two digits of Student ID	SET Number
Even , Even	SET-A
Even , Odd	SET-B
Odd , Even	SET-C
Odd , Odd	SET-D


SET-A

- 1(a).** The common-base amplifier is preferred for high-frequency signals when compared to the CE amplifier. Justify. CO1 Ev 01
- 1(b).** Evaluate the equations for voltage gain, current gain, input impedance, and output impedance for a BJT using low-frequency h-parameter model for CE configuration. CO3 Ev 03
- 1(c).** For the following network shown in “Fig: 1”, Determine the following parameters. CO2 Ev 02
- (a) r_e
 (b) Z_i & Z_o
 (c) A_v
- Consider r_o is very large.

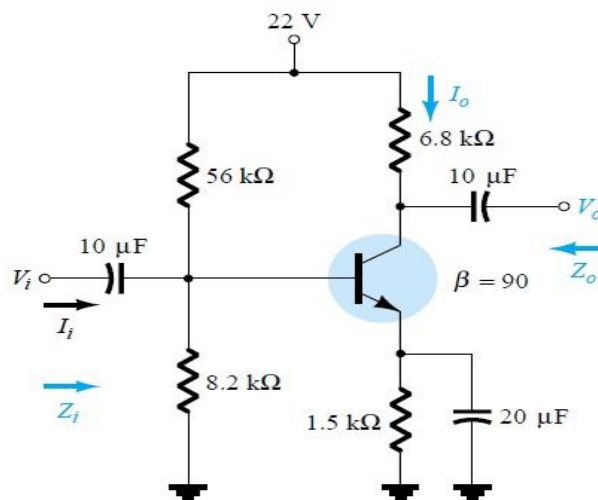


“Fig: 1” CE Amplifier circuit.

- 2(a). Why R_E is replaced by a constant current bias in a differential amplifier. Justify. **CO1 Ev 01**
- 2(b). Examine the circuit diagram for a differential amplifier using BJT's. Describe common mode and differential modes of working. **CO3 An 03**
- 2(c). Determine CMRR of differential amplifier with differential gain 300 and common-mode gain of 0.2. **CO2 Ev 02**
- 3(a). Create a relation between the three JFET parameters, μ , r_d , and g_m . **CO1 An 01**
- 3(b). Determine the following for the network of "Fig: 2", **CO2 Ev 02**
- V_{GSQ} .
 - I_{DQ} .
 - V_{DS} .
 - V_S .

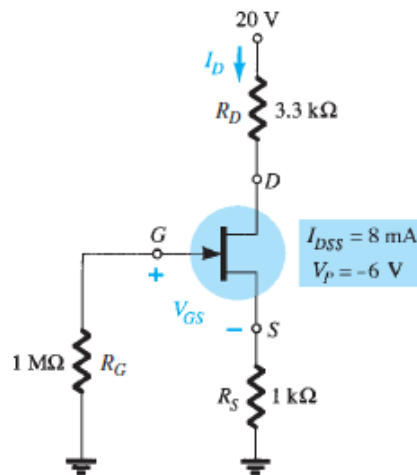

"Fig: 2" n-channel JFET (Self-Biased) circuit.

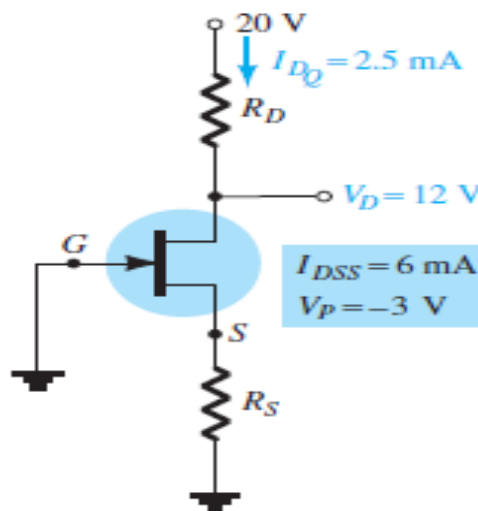- 3(c). For the network of "Fig: 3", the levels of V_{DQ} and I_{DQ} are specified. Determine the required values of R_D and R_S . What are the closest standard commercial values? **CO3 Ev 03**




"Fig: 3" n-channel JFET circuit.

- 4(a). Examine why Depletion MOSFET is commonly known as "Normally-ON" MOSFET? **CO1 Ap 01**
- 4(b). Compare enhancement and depletion modes of MOSFET with the help of its characteristics and construction. **CO1 An 03**
- 4(c). Derive the expression for transconductance of MOSFET. **CO1 An 02**


5(a). Explain the operation of CMOS as an inverter. CO1 U 02

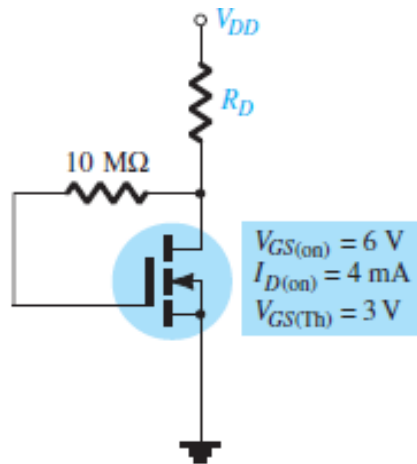5(b). The levels of V_{DS} and I_D are specified as $V_{DS} = (1/2) V_{DD}$ and $I_D = I_{D(on)}$ for the network shown in “Fig: 5”, Determine the levels of V_{DD} and R_D . CO2 Ev 02



“Fig: 4” n-channel Depletion MOSFET

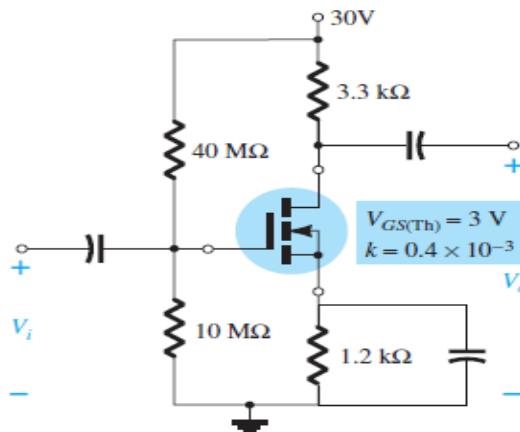5(c). Determine the output voltage (V_o) and Voltage gain (A_v) for an n-channel E-MOSFET is shown in “Fig: 5”, if $V_i = 0.8$ mV and $r_d = 40$ kΩ CO2 Ev 02



“Fig: 5” Voltage-divider biased n-channel E-MOSFET.

6. Viva-Quiz: The time of viva-quiz will be declared in google classroom. CO1

20

Prepared by,

Name: Md. Lokman Hossain

Designation: Lecturer

Department: EEE