

**International Islamic University Chittagong**  
**Department of Electrical and Electronic Engineering**

Final Assessment Autumn 2020	Program: B.Sc. Engg. (EEE)
Course Code: <b>EEE 2303</b>	Course Title: <b>Electrical Machine I</b>
Time: <b>5 hours</b> (Writing - <b>4 hours 30 minutes</b> + <b>30 minutes</b> submission time)	Full Marks: <b>50</b> (Written 30 + Viva/Viva-Quiz-20)

[Answer each of the questions (1-5) from the followings; Figures in the right margin indicate full marks.]

**SET-A**

<b>1(a).</b>	Which type of DC generator produce constant voltage? What is the condition for voltage buildup of that generator?	<b>CO2</b>	<b>U,U</b>	<b>2</b>																
<b>1(b).</b>	Classify the self-excited DC generator and draw the circuit diagram of each type.	<b>CO2</b>	<b>An</b>	<b>2</b>																
<b>1(c).</b>	A shunt generator delivers <b>XXX</b> A at <b>ZZZ</b> V and the resistance of shunt field and armature are $50\Omega$ and $0.03\Omega$ respectively. Calculate the generated emf. <b>XXX</b> is the 1 <sup>st</sup> three digit of your ID and <b>ZZZ</b> is the last three digits of your ID.	<b>CO3</b>	<b>E</b>	<b>2</b>																
<b>2(a).</b>	Draw the characteristics curve of the DC generator for i) No load Characteristics ii) External Characteristics.	<b>CO2</b>	<b>Ap</b>	<b>2</b>																
<b>2(b).</b>	Briefly describe the losses of DC generator.	<b>CO2</b>	<b>U</b>	<b>2</b>																
<b>2(c).</b>	The open circuit characteristics of a DC shunt generator driven at rated speed is as follow: <table border="1" style="margin: 10px auto; border-collapse: collapse;"> <tr> <td style="padding: 2px;">Field Amperes:</td> <td style="padding: 2px;">0.5</td> <td style="padding: 2px;">1.0</td> <td style="padding: 2px;">1.5</td> <td style="padding: 2px;">2.0</td> <td style="padding: 2px;">2.5</td> <td style="padding: 2px;">3.0</td> <td style="padding: 2px;">3.5</td> </tr> <tr> <td style="padding: 2px;">Induced Voltage:</td> <td style="padding: 2px;">60</td> <td style="padding: 2px;">120</td> <td style="padding: 2px;">138</td> <td style="padding: 2px;">145</td> <td style="padding: 2px;">149</td> <td style="padding: 2px;">151</td> <td style="padding: 2px;">152</td> </tr> </table> <p>If the resistance of the field circuit is adjusted to <b>yy</b> <math>\Omega</math>, calculate the open circuit voltage and load current when the terminal voltage is <b>rrr</b> V. Neglect armature reaction and assume an armature resistance of <math>0.1\Omega</math> <b>yy</b> is the last two digit of your ID and <b>rrr</b> is the 1<sup>st</sup> three digit of your ID.</p>	Field Amperes:	0.5	1.0	1.5	2.0	2.5	3.0	3.5	Induced Voltage:	60	120	138	145	149	151	152	<b>CO3</b>	<b>Ap</b>	<b>2</b>
Field Amperes:	0.5	1.0	1.5	2.0	2.5	3.0	3.5													
Induced Voltage:	60	120	138	145	149	151	152													
<b>3(a).</b>	A <b>xxx</b> V-shunt motor has armature resistance of $0.8\Omega$ and field resistance of <b>zzz</b> $\Omega$ . Determine the back emf when given an output of 7.46kW at 85% efficiency. <b>xxx</b> is the last three digit of your ID and <b>zzz</b> is the 1 <sup>st</sup> three digit of your ID.	<b>CO3</b>	<b>E</b>	<b>1.5</b>																
<b>3(b).</b>	How does back emf produce in a DC motor?	<b>CO2</b>	<b>U</b>	<b>1.5</b>																
<b>3(c).</b>	Which factors are influencing to the speed of DC motor? Explain the flux control methods of DC shunt motor with diagram.	<b>CO1</b>	<b>U</b>	<b>3</b>																
<b>4(a).</b>	Differentiate between Conduction motor and Induction motor.	<b>CO1</b>	<b>An</b>	<b>1</b>																
<b>4(b).</b>	Explain the production of rotating magnetic field in case of <b>three phase</b> supply in an induction motor.	<b>CO2</b>	<b>E</b>	<b>3</b>																
<b>4(c).</b>	A 4-pole 3-phase induction motor operates from a supply whose frequency is 60 Hz. Calculate (i) synchronous speed of the rotor, (ii) actual speed of the rotor when slip is <b>XX</b> %, (iii) frequency of the rotor current when speed is <b>ZZZ</b> rpm. <b>XX</b> is the 1 <sup>st</sup> two digit of your ID and <b>ZZZ</b> is the last three digits of your ID.	<b>CO3</b>	<b>Ap</b>	<b>2</b>																
<b>5(a).</b>	Draw the equivalent circuit of an induction motor by showing mechanical load as an electrical equivalent.	<b>CO2</b>	<b>Ap</b>	<b>2</b>																
<b>5(b).</b>	Show that the no load tests of induction motor is analogous to the open circuit test of transformer and the block rotor test is equivalent of short circuit test.	<b>CO1</b>	<b>Ap</b>	<b>3</b>																
<b>5(c).</b>	How $G_0$ and $B_0$ can be found from induction motor?	<b>CO2</b>	<b>U</b>	<b>1</b>																
<b>6.</b>	Viva/Viva-Quiz: The time of viva/viva-quiz will be declared in Google classroom.			<b>20</b>																