

International Islamic University Chittagong (IIUC)
Department of Computer and Communication Engineering
Final Examination

Program: B.Sc. Engg. (CCE)

Course Code: CCE – 1103

Total Marks: 50

Instructions:

1. Attempt 2 questions from part A and 3 questions from part B.
2. Make suitable assumptions wherever necessary.
3. Figures to the right indicate full marks.

Semester: Spring 2022


Course Title: Basic Electrical Engineering

Time: 2 Hours 30 Minutes


Part A

[Answer any two questions from following]

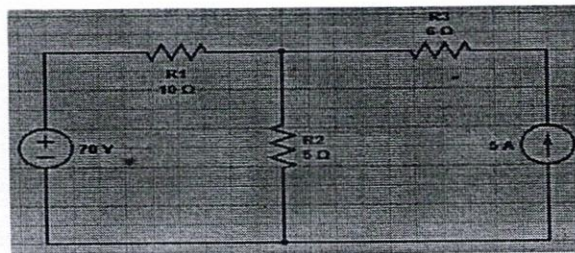
- Q1. (a) Calculate current flowing through each resistor and also calculate node voltage for the network. 5 CLO – 2



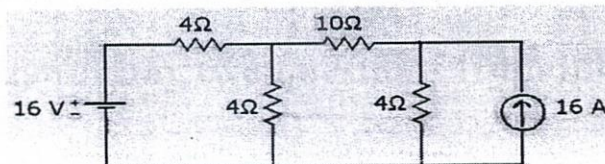- (b) Find the current through 10 Ω resistance in the given network by using superposition theorem. 5 CLO – 2




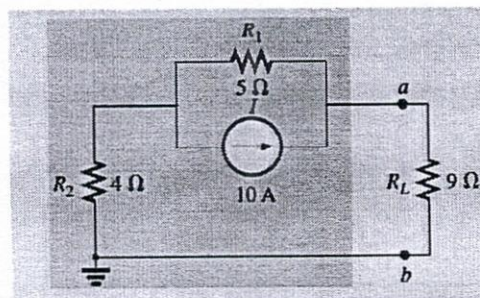- Q2. (a) Point out the differences between Thevenin's Theorem and Norton's Theorem. 2 CLO – 2
- (b) Find the Norton equivalent circuit for the network external to the 9 Ω resistor in Figure. 4 CLO – 2



- (c) In the circuit of figure, find the power loss in the 1Ω resistor by Thevenin's Theorem.

4 CLO - 2

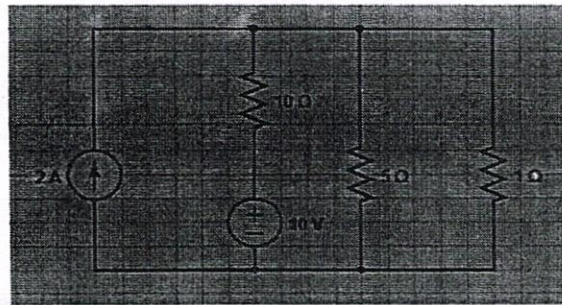


- Q3. (a) "Capacitor acts as an open circuit and Inductor acts as a short circuit in DC" justify the statement.
 (b) State Maximum Power Transfer Theorem and derive an expression for $P_{\max}$.
 (c) Find the value of R_L for maximum power transfer in the circuit of Figure. Find the maximum power.

3 CLO - 1

3 CLO - 2

4 CLO - 2

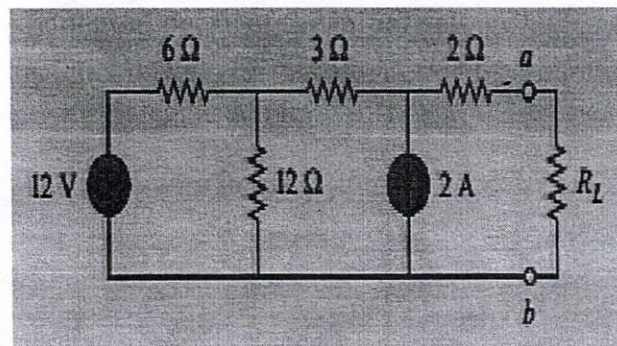

Part B


[Answer any three questions from the following]

- Q4. (a) Point out why First order circuits are named so.
 (b) Justify the statement with proper derivation - "Voltage response of the RC circuit is an exponential decay of the initial voltage".
 (c) The switch in the circuit of Figure has been closed for a long time. At $t = 0$, the switch is opened. Calculate $i(t)$ for $t > 0$.

2 CLO - 1


4 CLO - 2

4 CLO - 2

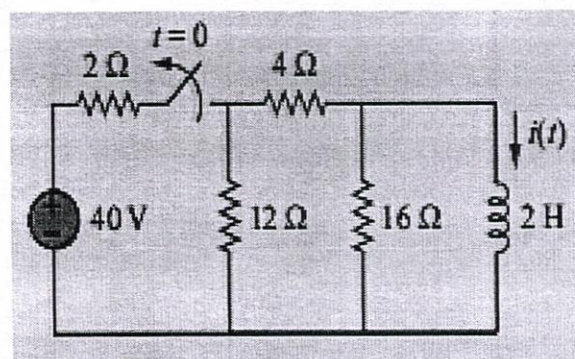


- Q5. (a) The switch in Figure has been in position A for a long time. At $t = 0$, the switch moves to B. Determine $v(t)$ for $t > 0$ and calculate its value at $t = 1$ s and 4 s.

5 CLO-2

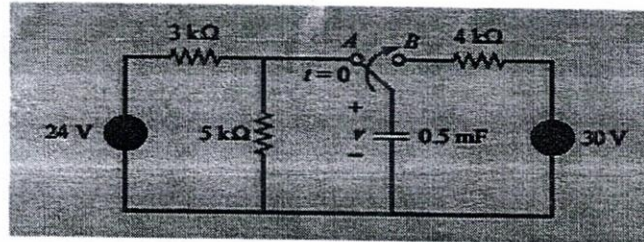

- (b) At $t = 0$, switch 1 in Figure is closed, and switch 2 is closed 4 s later. Find $i(t)$ for $t > 0$. Calculate i for $t = 2$ s and $t = 5$ s.

5 CLO-2

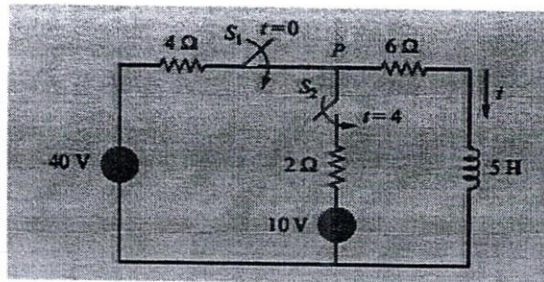

- Q6. (a) Define: Magnetic Flux, Permeability and Reluctance.
 (b) Explain the equivalent Ohm's law of Magnetic Circuit.
 (c) Explain Hysteresis curve with proper figure.


3 CLO-1

3 CLO-1

4 CLO-2

- Q7. (a) The circuit in Figure has reached steady state at $t = 0^-$. If the make before-break switch moves to position b at $t = 0$, calculate $i(t)$ for $t > 0$.

5 CLO-2

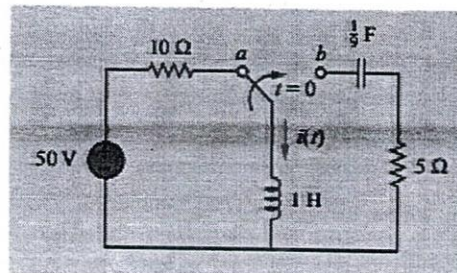

- (b) Find $v(t)$ for $t > 0$ in the RLC circuit of the Figure.

5 CLO-2

