

International Islamic University Chittagong (IIUC)
Department of Electronic and Telecommunications Engineering
Final Examination, Autumn- 2018

Course Code: ETE-1205
Full Marks: 50

Course Title: Electronic Devices
Time: 2 Hours 30 Minutes

(Figures in the margin indicate full marks)

Group-A

[Answer any two sets of the following questions]

1. (a) Justify the characteristics of transistor from its name. 2
(b) Why Transistor known as bipolar device? 3
(c) Draw and describe the input and output characteristics of common emitter configuration. 5
2. (a) What is faithful amplification? What are the conditions for achieving it? 2
(b) It is desired to set the operating point at 2V, 1mA by biasing a silicon transistor with collector feedback resistor R_B . If $\beta = 100$, find the value of R_B . 4

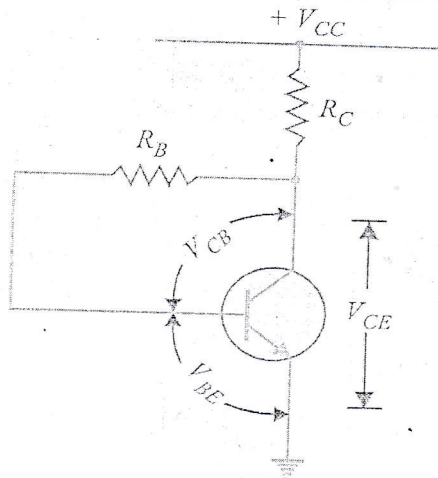


Figure 1

- (c) Figure 2 shows the voltage divider bias method. Draw the d.c. load line and determine the operating point. Assume the transistor to be of silicon. 4

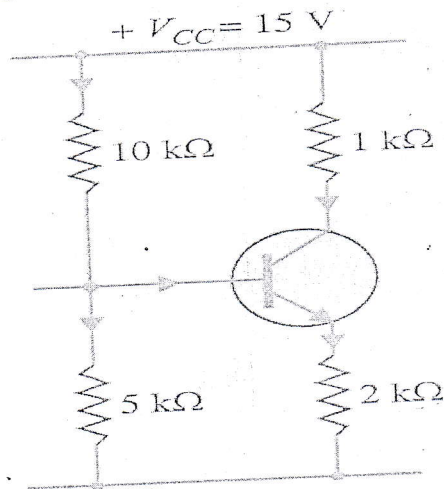


Figure 2

3. (a) What are the stability factors? If we have a lower value of stability factor, will the circuit be more sensitive to temperature variation? 2
- (b) How does emitter bias, voltage feedback bias physically offer higher stability than fixed bias configuration? Discuss by mentioning corresponding equations. 4
- (c) Determine the operating point for the following voltage divider bias configuration using exact and approximate analysis and comment on the results obtained: 4

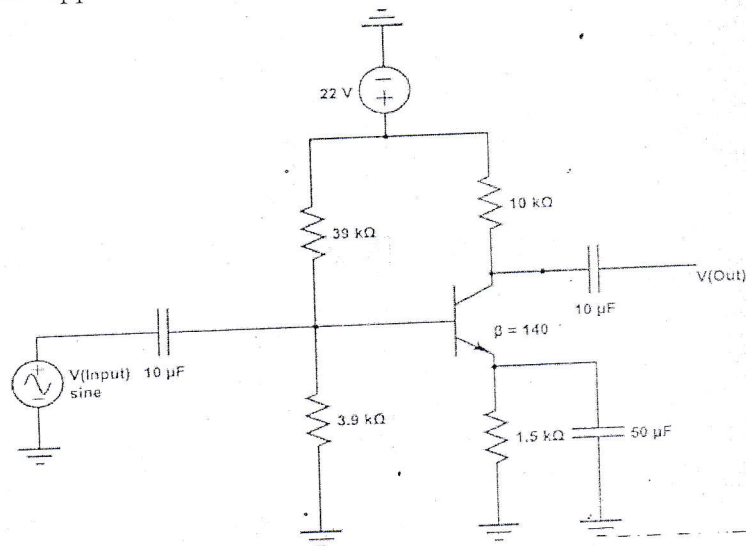


Figure 3

Group-B

[Answer any three sets of the following questions]

4. (a) Draw the ac equivalent network for the figure 4

4

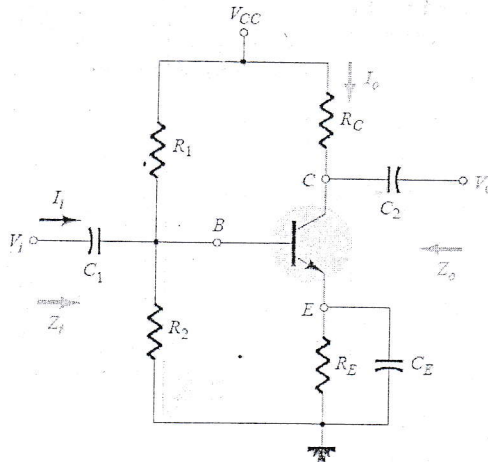


Figure 4

- (b) For the network of Figure 5: (i) Determine r_e . (ii) Find Z_i (with $r_o = \alpha \Omega$). (iii) Calculate Z_o (with $r_o = \alpha \Omega$). (iv) Determine A_v (with $r_o = \alpha \Omega$). (v) Find A_i (with $r_o = \alpha \Omega$). (vi) Repeat parts (c) through (e) including $r_o = 50 \text{ k}\Omega$ in all calculations and compare results.

6

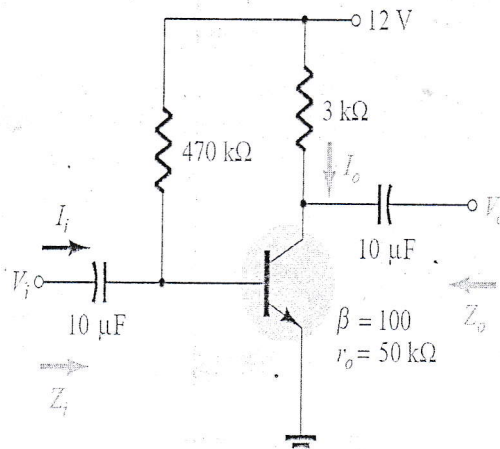


Figure 5

5. (a) What is the basic difference between Depletion and enhancement type MOSFET? 2
 (b) Why MOSFET is named so? Describe in brief the operation of NMOS with its transfer characteristics. (Draw necessary Figures) 3
 (c) Determine for the figure 6: V_{GS} (Quiescent), I_D (Quiescent), V_{DS} , V_D , V_G and V_S . 3

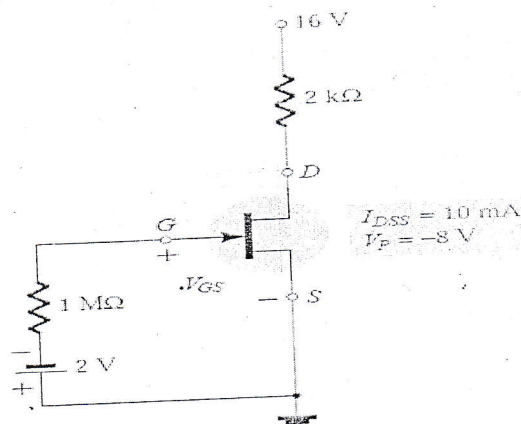


Figure 6

6. (a) Derive the hybrid parameter of an amplifier. 2
 (b) Find out the hybrid parameter of CB configuration and its application in a circuit. 3
7. (a) What is the basic difference between D-MOSFET and E-MOSFET? 2
 (b) Determine the following for the network of Figure 7. (i) I_{DQ} and V_{GSQ} , (ii) V_D . 4

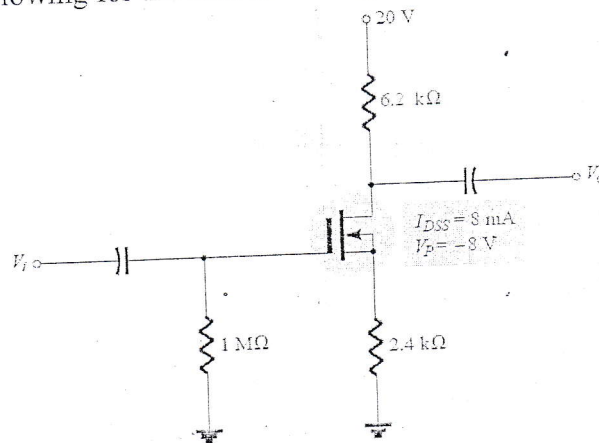


Figure 7

- (c) Explain how a CMOS work as an inverter. 4